

# CHAPTER 6. COMBINATIONAL CIRCUITS

---

## ❖ Adder

- Half Adder
- Full Adder
- Parallel Adder

## ❖ Comparator

## ❖ Decoder

## ❖ Encoder

# Half Adder

---

## Half Adder (HA)

Binary addition, as previously mentioned, works as follows:

$$0+0 = 0 \text{ (sum=0, carry=0)}$$

$$0+1 = 1 \text{ (sum=1, carry=0)}$$

$$1+0 = 1 \text{ (sum=1, carry=0)}$$

$$1+1 = 10 \text{ (sum=0, carry=1)}$$

A half adder is a circuit designed to perform one-bit addition. It is a combinational circuit that takes two 1-bit numbers as input and provides two outputs: the sum and the carry.


# Half Adder

Truth table for a half adder is shown below.


A B	Sum	Carry
0 0	0	0
0 1	1	0
1 0	1	0
1 1	0	1

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = A.B$$

 

Logic diagram for a half adder

 

Block diagram for a half adder

# Full Adder

## Full Adder (FA)

A full adder is a combinational circuit with three inputs (two 1-bit binary numbers and a carry-in) and two outputs (sum and carry-out). Unlike a half adder, the full adder includes an additional input for the carry-in.

The truth table for a full adder is shown below.

Inputs			Outputs	
A	B	ci	Sum	co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$\begin{aligned}\text{Sum} &= A'.B'.ci + A'.B.ci' + A.B'.ci' + A.B.ci \\ &= ci.(A'.B' + A.B) + ci'.(A'.B + A.B') \\ &= ci.(A \oplus B)' + ci'.(A \oplus B) \\ &= A \oplus B \oplus ci\end{aligned}$$

$$\begin{aligned}co &= A'.B.ci + A.B'.ci + A.B.ci' + A.B.ci \\ &= ci.(A \oplus B) + A.B\end{aligned}$$


# Full Adder

$$\text{Sum} = A \oplus B \oplus ci$$

$$co = ci.(A \oplus B) + A.B$$

 


Logic diagram for a full adder

 

Block diagram for a full adder

 A full adder can be constructed using two half adders and an OR gate, as shown below:



In a half adder  
Carry =  $A.B$   
Sum =  $A \oplus B$

# Parallel Adder


## Parallel Binary Adder

We use half adders and full adders to add 1-bit binary numbers. To add binary numbers with more than one bit, **parallel adders** are used. A parallel adder is implemented by cascading multiple full adders.

For instance, a **4-bit parallel adder** is created by connecting four full adders in sequence:


- The **carry-out** of each full adder is connected to the **carry-in** of the next full adder.
- The **carry-in** of the first full adder (handling the least significant bits, LSBs) is set to 0.
- The **carry-out** of the last full adder (handling the most significant bits, MSBs) becomes the final carry output of the parallel adder.

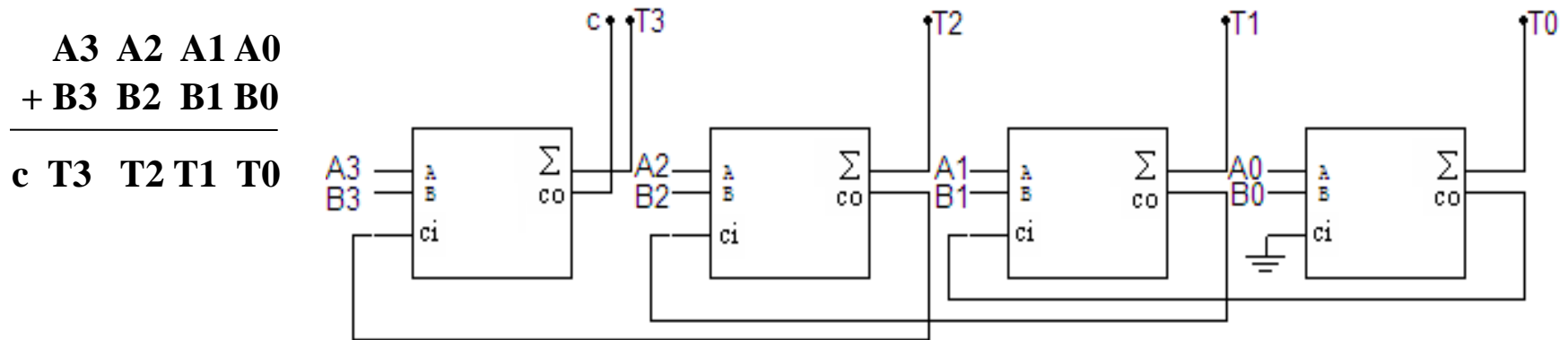This arrangement allows efficient addition of multi-bit binary numbers.


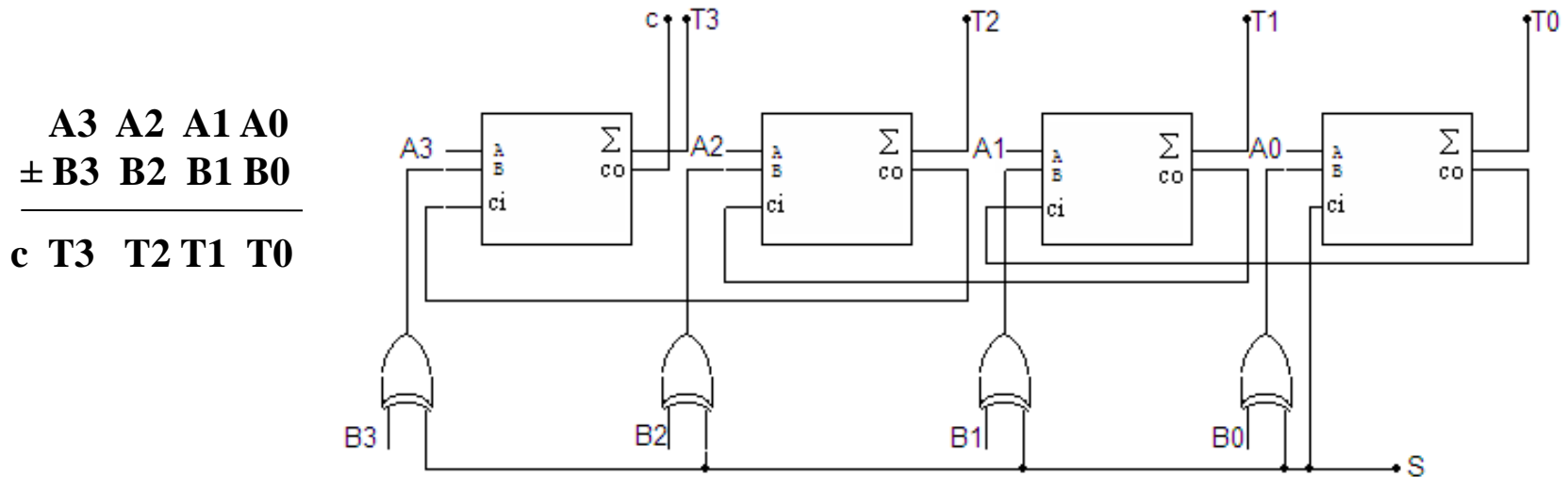
# Parallel Adder

Binary subtraction can be performed using two's complement. The circuit shown below handles both addition and subtraction. To subtract a binary number, we first convert the number  $(B3B2B1B0)_2$  to its two's complement by inverting all its bits and adding 1 to the result. The inversion of the bits is achieved using XOR gates, and the addition of 1 is done by providing a carry-in of 1 to the first full adder. The circuit then uses this two's complement to perform subtraction alongside addition, enabling it to handle both operations.




When  $S = 0$ , the circuit performs addition.

When  $S = 1$ , the circuit performs subtraction.
 
# Comparator

Comparators are used to compare the magnitude of two binary numbers. To detect if two numbers are equal, we use XOR or XNOR gates. For example, to compare two 2-bit numbers,  $A_3A_2A_1A_0$  and  $B_3B_2B_1B_0$ , the circuit shown below can be used.



This circuit outputs 1 when the two numbers are equal and outputs 0 when they are different. The same concept can be extended to compare N-bit numbers by expanding the circuit accordingly.



# Comparator

---

For example, if we want to compare the magnitudes of two 4-bit numbers ( $A_3A_2A_1A_0$  and  $B_3B_2B_1B_0$ ), we can write the following expressions:

- If  $A_3=1$  and  $B_3=0$ , then  $A>B$ ,
- If  $A_3=0$  and  $B_3=1$ , then  $A<B$ ,
- If  $A_3=B_3$ , we need to check the less significant bits.

The following equalities can be written:

$$\text{Output (A>B)} = A_3.B_3' + (A_3 \otimes B_3).A_2.B_2' + (A_3 \otimes B_3).(A_2 \otimes B_2).A_1.B_1' + (A_3 \otimes B_3).(A_2 \otimes B_2).(A_1 \otimes B_1).A_0.B_0'$$

$$\text{Output (A<B)} = A_3'.B_3 + (A_3 \otimes B_3).A_2'.B_2 + (A_3 \otimes B_3).(A_2 \otimes B_2).A_1'.B_1 + (A_3 \otimes B_3).(A_2 \otimes B_2).(A_1 \otimes B_1).A_0'.B_0$$

$$\text{Output (A=B)} = (A_3 \otimes B_3).(A_2 \otimes B_2).(A_1 \otimes B_1).(A_0 \otimes B_0)$$

# Decoder

Decoders are combinational circuits with  $n$  inputs and at most  $2^n$  outputs. The input is a binary number, and the active output corresponds to its decimal value.

The truth table of a  $2 \times 4$  decoder is shown below.


$X_1 X_0$	$Y_0$	$Y_1$	$Y_2$	$Y_3$
0 0	1	0	0	0
0 1	0	1	0	0
1 0	0	0	1	0
1 1	0	0	0	1

$$Y_0 = X_1' \cdot X_0'$$

$$Y_1 = X_1' \cdot X_0$$

$$Y_2 = X_1 \cdot X_0'$$

$$Y_3 = X_1 \cdot X_0$$

 

Block diagram of a  $2 \times 4$  decoder

# Decoder



In decoders, an enable (EN) input can also be used. When  $EN = 1$ , the decoder operates normally, but when  $EN = 0$ , the outputs are inactive (all outputs are 0).

$$Y_0 = X_1' \cdot X_0'$$

$$Y_1 = X_1' \cdot X_0$$

$$Y_2 = X_1 \cdot X_0'$$

$$Y_3 = X_1 \cdot X_0$$

  


# Decoder

Decoders can be used to implement logical functions. Each output of a decoder represents a minterm.

In general, a logical expression with  $n$  inputs and  $m$  outputs can be implemented using an  $n \times 2^n$  decoder and  $m$  OR gates.

 **Example:** Let's implement  $f(x,y,z) = \Sigma(0,1,3,5)$  and  $g(x,y,z) = \Sigma(1,6,7)$  with a decoder.



# Encoder

Encoders are combinational circuits that perform the reverse operation of decoders. Generally, they have  $n$  outputs and at most  $2^n$  inputs. Under normal conditions, only one of the inputs should be 1. In this case, the circuit produces a binary code at the output, indicating which input is 1.

The truth table for a 4-input, 2-output encoder is as follows:



$D_0$	$D_1$	$D_2$	$D_3$	$Z_1$	$Z_0$
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

Since only one input is allowed to be 1 at the same time, we can treat cases where multiple inputs are 1 simultaneously as "don't care" conditions when calculating the  $Z_1$  and  $Z_0$  outputs using Karnaugh maps.

$$Z_1 = D_2 + D_3$$

$$Z_0 = D_1 + D_3$$

  
$$NI = D_0' . D_1' . D_2' . D_3' \text{ (No Input)}$$




# Encoder

In some cases, it may not be possible for only one input of the encoder to be 1 at a time. To handle such situations, priority encoders have been developed. An example implementation for 4 inputs and 3 outputs is shown below, where the priority order is from  $D_3$  to  $D_0$ .

$D_0$	$D_1$	$D_2$	$D_3$	$Z_1$	$Z_0$	NI
0	0	0	0	x	x	1
1	0	0	0	0	0	0
x	1	0	0	0	1	0
x	x	1	0	1	0	0
x	x	x	1	1	1	0

 

$$Z_1 = D_2 + D_3$$

 

$$Z_0 = D_3 + D_2' \cdot D_1$$


$$NI = D_0' \cdot D_1' \cdot D_2' \cdot D_3'$$

# Encoder

$$Z_1 = D_2 + D_3$$

$$Z_0 = D_3 + D_2' \cdot D_1$$
 
$$NI = D_0' \cdot D_1' \cdot D_2' \cdot D_3' = (D_0 + D_1 + D_2 + D_3)'$$



Logic diagram for a 4×2 priority encoder